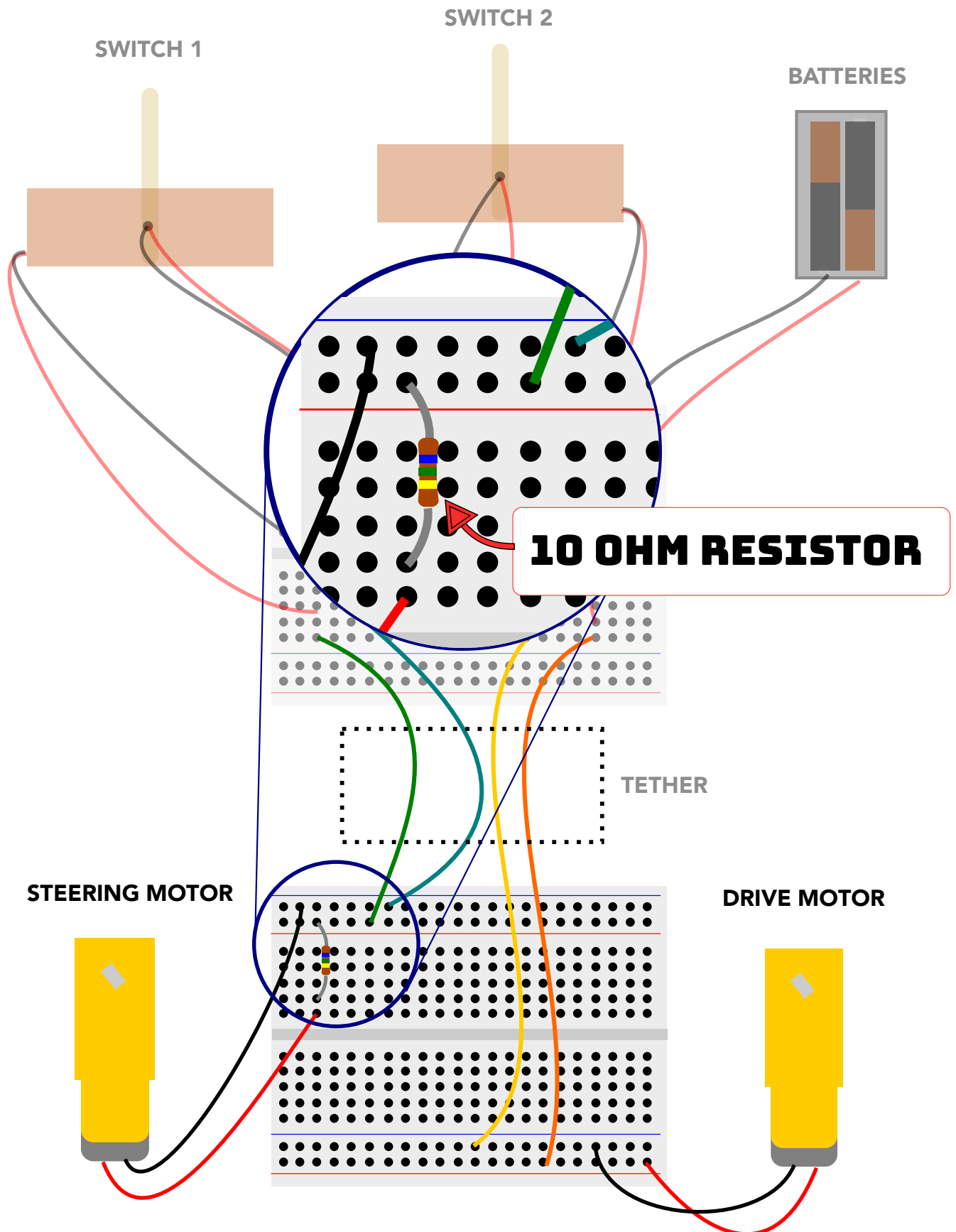




This is a suggested wiring diagram only. You do not have to use the breadboard holes indicated here, as long as the wires make the correct connections.

STEERING RESISTOR